



GEBZE TECHNICAL
UNIVERSITY
ELECTRONIC
ENGINEERING


ELEC-227

Circuit Theory II Project

Prepared by
2) 200102002043 – Senanur Ağaç

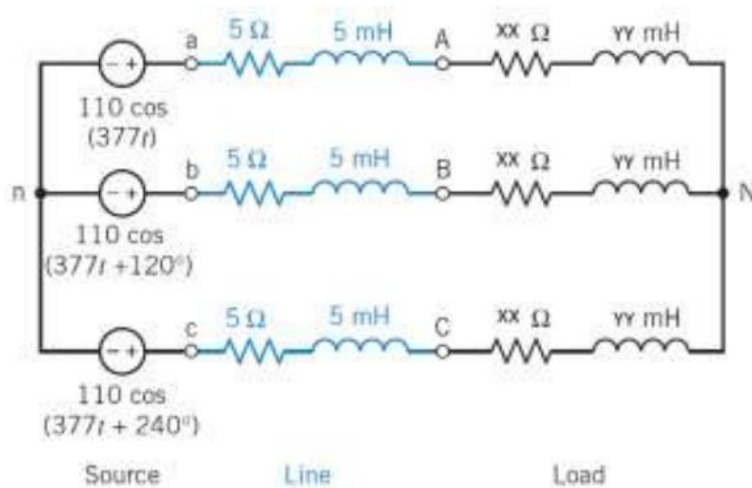1. Answer the following questions by assigning the first two digits and the last two digits of your school number (XX.....YY) to the resistance (XX) and reactance (YY) of load, respectively in the balanced three-phase circuit shown in Figure 1.

- Determine the power delivered to the load (apparent power, complex power, active and reactive power).
- Determine the each line current (I_a , I_b , I_c).
- Determine the each line to neutral voltage (V_{AN} , V_{BN} , V_{CN}).
- Determine the compensating impedance to the load to adjust the power factor to 1.
- Determine items a, b and c after compensation.
- Make comparisons and comments on items a, b, c, and e. Verify with any application (i.e. PSpice, Multisim, etc).



XX = 20 → First two digits of school number

YY = 43 → Last two digits of school number

Figure 1

SOLUTION :

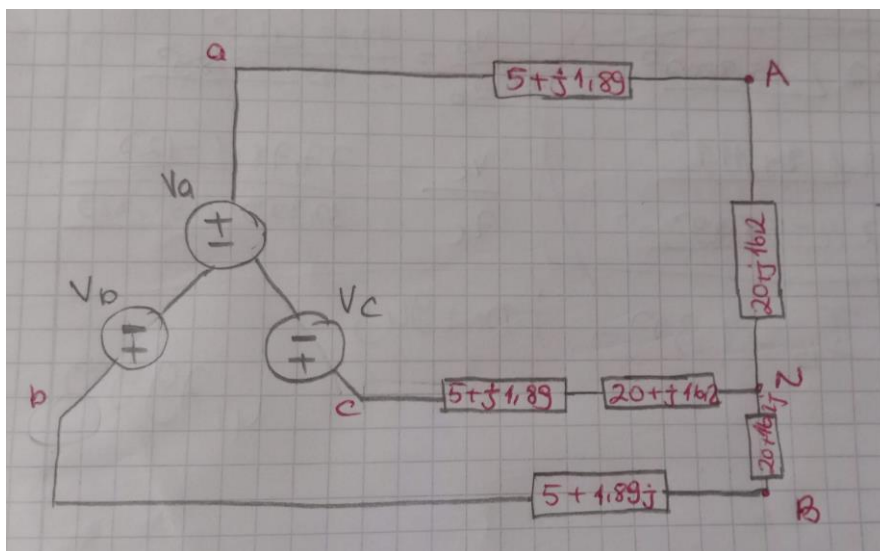


Figure 2

$$V_a = 110 \cdot \cos(377t) = 77,78 \angle 0^\circ V_{rms}$$

$$V_b = 110 \cdot \cos(377t + 120) = 77,78 \angle 120^\circ V_{rms}$$

$$V_c = 110 \cdot \cos(377t + 240) = 77,78 \angle -120^\circ V_{rms}$$

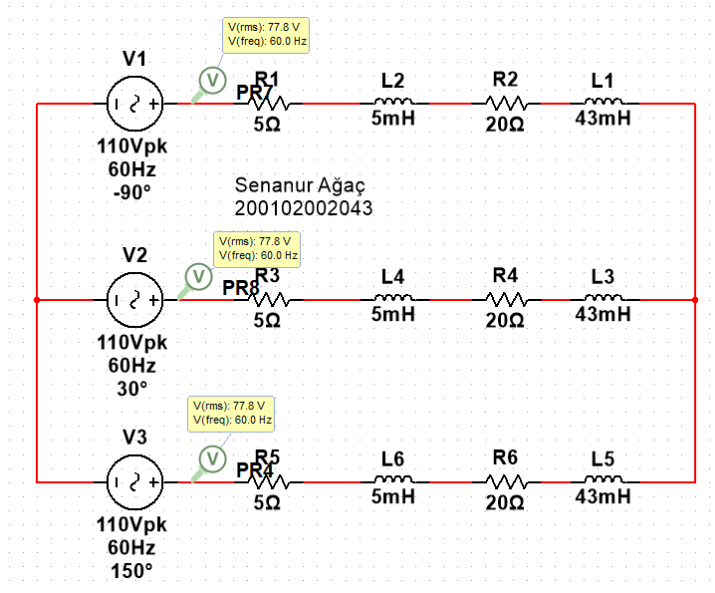


Figure 3

$$Z_{LINE} = 5\Omega + 5mH = 5\Omega + j\omega L = 5 + j1,89 \Omega$$

$$Z_{LOAD} = 20\Omega + 43mH = 20\Omega + j\omega L = 20 + j16,2 \Omega$$

$$Z_{sum} = 25 + j18,09 \Omega$$

$$I_A = \frac{V_a}{Z_{sum}} = \frac{77,78 \angle 0^\circ}{25 + j18,09 \Omega} = 2,52 \angle -35,889^\circ A$$

$$I_B = \frac{V_b}{Z_{sum}} = \frac{77,78 \angle 120^\circ}{25 + j18,09 \Omega} = 2,52 \angle 84,111^\circ A$$

$$I_C = \frac{V_c}{Z_{sum}} = \frac{77,78 \angle -120^\circ}{25 + j18,09 \Omega} = 2,52 \angle -155,89^\circ A$$

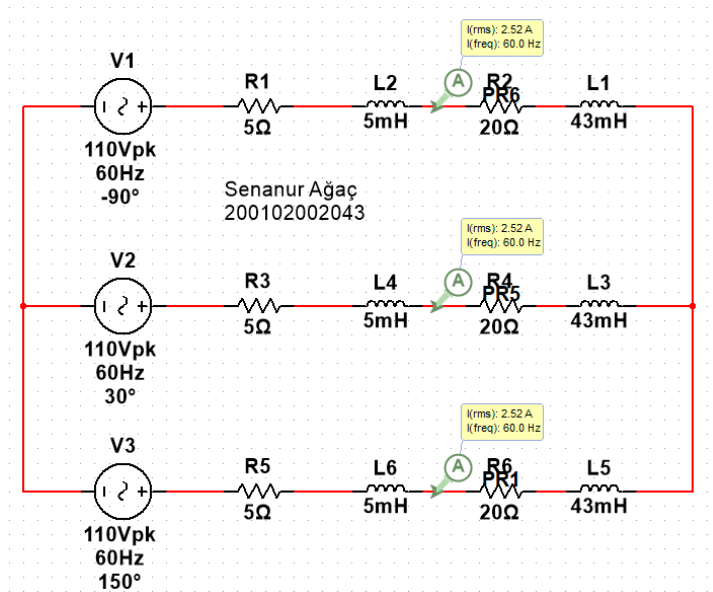


Figure 4 : Simulation

It should be $I_A + I_B + I_C = 0$. Let's verify this ;

$$(2,52 \angle -35,889^\circ \text{ A}) + (2,52 \angle 84,111^\circ \text{ A}) + (2,52 \angle -155,89^\circ \text{ A}) = 0.00001 + j0.00004$$

It is very close to 0 due to the rounding in mathematical calculations.

$$V_{AN} = I_A * Z_{LOAD} = 2,52 \angle -35,889^\circ \text{ A} * (20 + j16,2 \Omega) = 64,64 \angle 3,985^\circ \text{ V}$$

$$V_{BN} = I_B * Z_{LOAD} = 2,52 \angle 84,111^\circ \text{ A} * (20 + j16,2 \Omega) = 64,86 \angle 123,12^\circ \text{ V}$$

$$V_{CN} = I_C * Z_{LOAD} = 2,52 \angle -155,89^\circ \text{ A} * (20 + j16,2 \Omega) = 64,859 \angle -116,88^\circ \text{ V}$$

Figure 5: Simulation

$$\text{Apparent Power} = V_{AN} * I_{LOAD} = 64,64 * 2,52 = 162,8 \text{ VA}$$

$$\text{Complex Power} = V_{AN} * I_{LOAD}^* = 64,64 \angle 3,118^\circ * 2,52 \angle 35,889^\circ = 162,89 \angle 39,007^\circ$$

$$163,44 \angle 39,007^\circ = 127.004 + j102.87 \text{ VA}$$

Active
power
Rective
power

$$\text{Active Power} = 127.004 \text{ W}$$

$$\text{Reactive Power} = 102.87 \text{ VAR}$$

$$\text{Power Factor} = \text{Active Power} / \text{Reactive Power} = 127.004 / 162.8 = 0.79$$


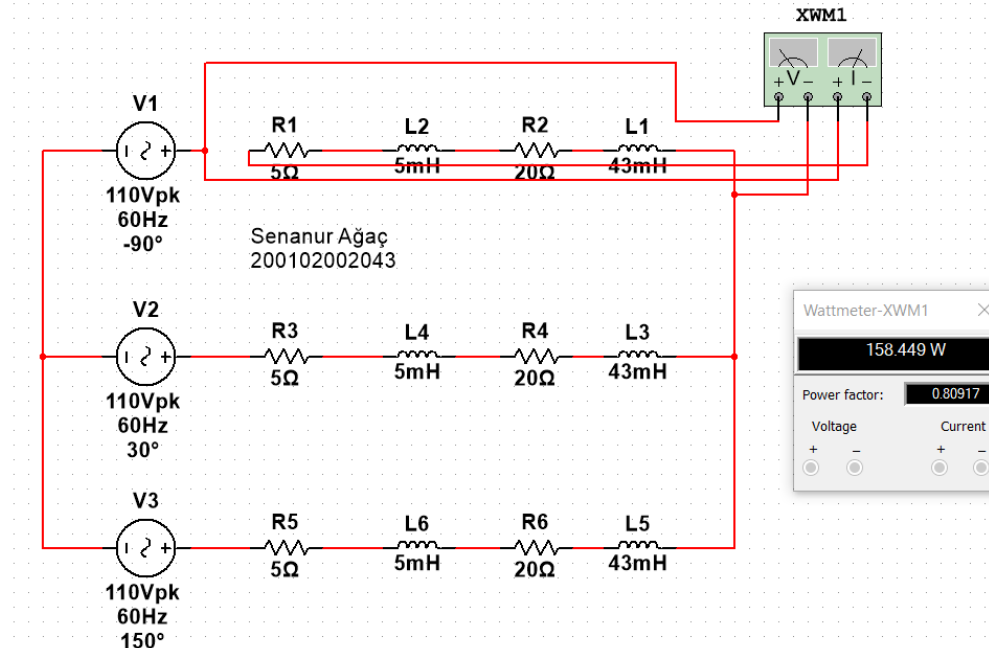


Figure 6 : Simulation

e)

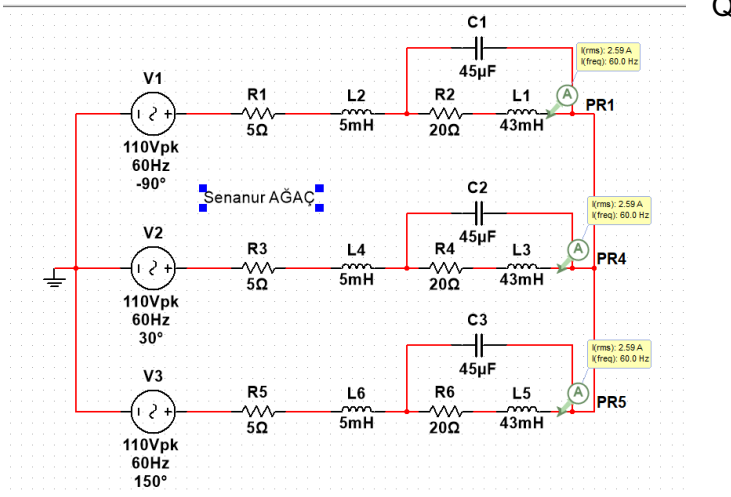

$$W = V_{rms}^2 / (w \cdot c) \rightarrow 102.87 = (77.78)^2 / (1/377 \cdot C) \rightarrow C = 45 \mu F$$

$$Z_c = j58.9 \rightarrow j59$$


$$Z_{line} = 5 + j1.89 \Omega$$

$$Z_{load} = 20 + 16.2 \Omega$$

$$Z_{line} + Z_{load} = 25 + 18.09$$

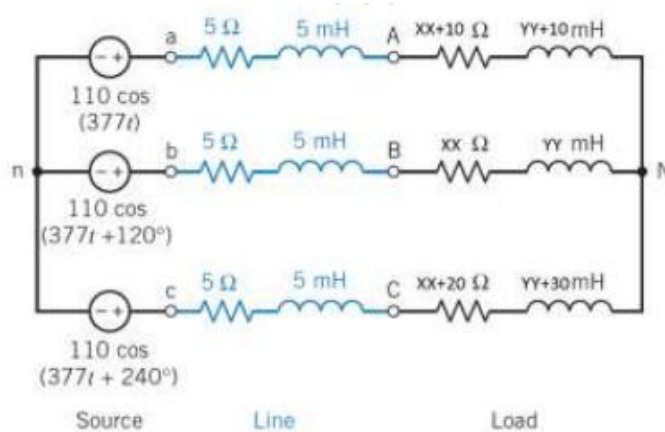2. Answer the following questions by assigning the first two digits and the last two digits of your school number (XX.....YY) to the resistance (XX) and reactance (YY) of each phase load, respectively in the unbalanced three-phase circuit shown in Figure 2.

- Determine the power delivered to the unbalanced load (apparent power, complex power, active and reactive power).
- Determine the each line current (I_a , I_b , I_c).
- Determine the each line to neutral voltage (V_{AN} , V_{BN} , V_{CN}).
- Determine the compensating impedance to the each phase load to adjust the power factor to 1.
- Determine items a, b and c after compensation. f) Make comparisons and comments on items a, b, c, and e.



XX = 20 → First two digits of school number

YY = 43 → Last two digits of school number

Figure 2

$$\begin{aligned} V_a &= 110 \cdot \cos(377t) &= 77,78 \angle 0^\circ V_{\text{rms}} \\ V_b &= 110 \cdot \cos(377t + 120) &= 77,78 \angle 120^\circ V_{\text{rms}} \\ V_c &= 110 \cdot \cos(377t + 240) &= 77,78 \angle -120^\circ V_{\text{rms}} \end{aligned}$$

$$Z_{\text{load-a}} = 30 + j \cdot 377 \cdot (53 \cdot 10^{-3}) = 30 + j19.9 \, \Omega$$

$$Z_{\text{load-b}} = 20 + j \cdot 377 \cdot (43 \cdot 10^{-3}) = 20 + j16.2 \, \Omega$$

$$Z_{\text{load-c}} = 40 + j \cdot 377 \cdot (73 \cdot 10^{-3}) = 40 + j27.5 \, \Omega$$

$$Z_{\text{line-a}} = Z_{\text{line-b}} = Z_{\text{line-c}} = 5 + j1,89 \, \Omega$$

$$I_A = \frac{V_a}{Z_{\text{line-a}} + Z_{\text{load-a}}} = \frac{77,78 \angle 0^\circ}{35 + j21,79 \, \Omega} = 1,886 \angle -31,905^\circ \, \text{A}$$

$$I_B = \frac{V_b}{Z_{\text{line-b}} + Z_{\text{load-b}}} = \frac{77,78 \angle 120^\circ}{25 + j18,09 \, \Omega} = 2,52 \angle 84,126^\circ \, \text{A}$$

$$I_c = \frac{V_c}{Z_{line-c+load-c}} = \frac{77,78 \angle -120^\circ}{45 + j29,39 \Omega} = 1,447 \angle -153,149^\circ \text{ A}$$

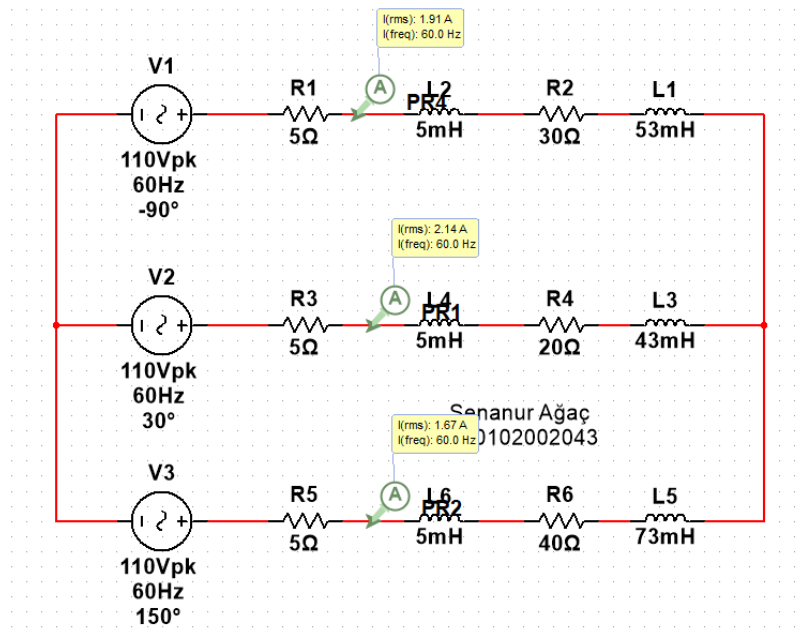


Figure 7 : Simulation